# CPLD 設計作業

# 銘傳大學電腦與通訊工程系

| 班 級     | 電通二乙             |
|---------|------------------|
| 組 別     | 第 27 組           |
| 組員姓名/學號 | 陳韋澔/05050032     |
| 組員姓名/學號 | 陳奕璁/05050536     |
| 作業撰寫人   | 陳韋澔/05050032     |
| 授課教師    | 陳慶逸              |
| 實習成果    | 本次應繳作業共2 題,完成2 題 |
| 時 間     | 2017/12/29       |

#### 第一題

□ 問題描述: 驗證 PWM 程式,利用 SW[7]-SW[0]控制 LEDG[0]的輸出亮度。

### PWM 程式

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
entity pwm is
port(
                                                  --系統頻率
      CLOCK_50: in std_logic;
             : in std_logic_vector(7 downto 0); --PWM 控制訊號
      SW
      pwm: out std_logic
                                               --PWM 訊號輸出
    );
end pwm;
architecture a of pwm is
  signal B:std_logic_vector(7 downto 0);
begin
  ----- 下數計數器 -----
  process(CLOCK_50)
  begin
    if CLOCK_50'event and CLOCK_50='1' then
```

成果: https://www.youtube.com/watch?v=S7YRiCqYM-M

# 第二題

題目:設計一個自動切換上下數的計數器 (00000000->00000001->...->11111111->11111110->....00000000->...),用以控制 pwm 輸出的明亮變化。 頻率器

```
process(clockIN)
variable counter, divisor2: integer range 0 to divisor;
begin
  divisor2:=divisor/2;
----- up counter -----
    if (clockIN 'event and clockIN ='1') then
       if counter = divisor then
          counter := 1;
       else
          counter := counter + 1;
       end if;
     end if;
  ---- clk generator ----
    if (clockIN 'event and clockIN ='1') then
       if (( counter= divisor2) or (counter = divisor))then
         PULSE <= not PULSE ;</pre>
       end if;
     end if;
    clockOUT <= PULSE;</pre>
  end process;
end arch
```

# 大頻率器

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;
```

```
entity freq_gene is
port(
     clk : in std_logic;
     f1Hz,f5Hz,f10Hz,f30Hz,f60Hz,f100Hz: out std_logic
    );
end freq_gene;
architecture arch of freq_gene is
component slowCLK
  generic(divisor:integer:=8);
port( clockIN : in std_logic;
      clockOUT: out std_logic);
end component;
begin
u1: slowCLK
    generic map(50000000)
                              --1Hz
    port map(clk,f1Hz);
u2: slowCLK
    generic map(1000000)
                              --5Hz
    port map(clk,f5Hz);
u3: slowCLK
    generic map(5000000)
                           --10Hz
    port map(clk,f10Hz);
u4: slowCLK
```

```
generic map(1666666) --30Hz

port map(clk,f30Hz);

u5: slowCLK

generic map(833333) --60Hz

port map(clk,f60Hz);

u6: slowCLK

generic map(500000) --100Hz

port map(clk,f100Hz);

end arch;
```

#### 上下數計數器

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_UNSIGNED.ALL;
ENTITY UP_COUNTER is
PORT( CLK: INSTD_LOGIC;
Q : OUT STD_LOGIC_VECTOR(7 DOWNTO 0));
END UP_COUNTER;
ARCHITECTURE a OF UP_COUNTER IS
SIGNAL QN : STD_LOGIC_VECTOR(7 DOWNTO 0);
SIGNAL SN: STD_LOGIC;
BEGIN
   PROCESS (CLK)
   BEGIN
      IF CLK'event AND CLK='1' THEN
     IF SN='0' THEN
```

```
IF QN="11111111" THEN
       SN<='1';
      ELSE
       QN \le QN+1;
      END IF;
      ELSE
      IF QN="00000000" THEN
       SN<='0';
      ELSE
       QN \le QN-1;
      END IF;
      END IF;
      END IF;
   END PROCESS;
   Q \le QN;
END a;
```

# PWM 程式


```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
entity pwm is
port(

CLOCK_50: in std_logic; --条統頻率
```

```
: in std_logic_vector(7 downto 0); --PWM 控制訊號
      SW
      pwm: out std_logic
                                              --PWM 訊號輸出
    );
end pwm;
architecture a of pwm is
  signal B:std_logic_vector(7 downto 0);
begin
  ----- 下數計數器 -----
  process(CLOCK_50)
  begin
    if CLOCK_50'event and CLOCK_50='1' then
      B \le B-1;
    end if;
  end process;
  --比較器
  pwm \le 1' when SW > B else '0';
end a;
```
 
#### 成果:

https://www.youtube.com/watch?v=eUaousXJSPY



#### 影片連結: