


CPLD 設計作業

銘傳大學電腦與通訊工程系


班 級	電通二乙
組 別	第 27 組
組員姓名/學號	陳韋濤/05050032
組員姓名/學號	陳奕璉/05050536
作業撰寫人	陳韋濤
授課教師	陳慶逸
實習成果	本次應繳作業共 <u>2</u> 題，完成 <u>2</u> 題
時 間	2017/12/22

第一題

 問題描述：請分別設定掃描頻率為 1Hz, 10Hz, 30Hz, 60Hz, 100Hz，觀察七段顯示器的計數結果有何不同？



模擬結果：

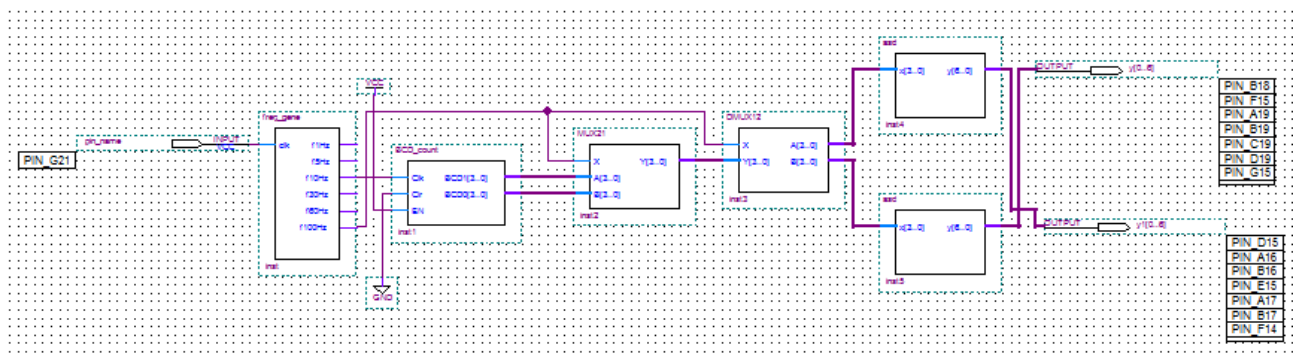

多工掃描，100Hz 計數器

<https://www.youtube.com/watch?v=WaJmMcV2WIs>

第二題

問題： 利用 DE0 實現一個多工掃描式的 4 位數 BCD 計數器

程式碼：

七段顯示器

```
library ieee;
use ieee.std_logic_1164.all;

entity asd is
    port(    x:in std_logic_vector(3 downto 0);
           y:out std_logic_vector(6 downto 0));
end asd;

architecture a of asd is
    begin
        with x select
            y <= "0000001" when "0000",
                "1001111" when "0001",
                "0010010" when "0010",
                "0000110" when "0011",
                "1001100" when "0100",
                "0100100" when "0101",
                "0100000" when "0110",
                "0001111" when "0111",
                "0000000" when "1000",
                "0000100" when "1001",
                "0001000" when "1010",
```

```

        "1100000" when "1011",
        "0110001" when "1100",
        "1000010" when "1101",
        "0110000" when "1110",
        "1111111" when others;

end a;

```

除頻

```

library ieee;
use ieee.std_logic_1164.all;

entity asd is
    port(   x:in std_logic_vector(3 downto 0);
           y:out std_logic_vector(6 downto 0));
end asd;

architecture a of asd is
    begin
        with x select
            y <= "0000001" when "0000",
                "1001111" when "0001",
                "0010010" when "0010",
                "0000110" when "0011",
                "1001100" when "0100",
                "0100100" when "0101",
                "0100000" when "0110",
                "0001111" when "0111",
                "0000000" when "1000",

```

```
"0000100" when "1001",  
"0001000" when "1010",  
"1100000" when "1011",  
"0110001" when "1100",  
"1000010" when "1101",  
"0110000" when "1110",  
"1111111" when others;
```

```
end a;
```

多功除頻

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_unsigned.all;  
use ieee.std_logic_arith.all;  
  
entity freq_gene is  
port(  
    clk : in std_logic;  
    f1Hz,f5Hz,f10Hz,f30Hz,f60Hz,f200Hz: out std_logic  
);  
end freq_gene;  
  
architecture arch of freq_gene is  
  
component slowCLK  
    generic(divisor:integer:=8);  
port( clockIN : in  std_logic;
```

```

        clockOUT: out std_logic);
end component;

begin

u1: slowCLK
    generic map(50000000)    --1Hz
    port map(clk,f1Hz);
u2: slowCLK
    generic map(10000000)    --5Hz
    port map(clk,f5Hz);
u3: slowCLK
    generic map(5000000)     --10Hz
    port map(clk,f10Hz);
u4: slowCLK
    generic map(1666666)     --30Hz
    port map(clk,f30Hz);
u5: slowCLK
    generic map(833333)      --60Hz
    port map(clk,f60Hz);
u6: slowCLK
    generic map(250000)      --100Hz
    port map(clk,f200Hz);
end arch;

```

BCD_COUNT

```

LIBRARY ieee ;

```

```
USE ieee.std_logic_1164.all ;
```

```
USE ieee.std_logic_unsigned.all ;
```

```
ENTITY BCD_count IS
```

```
PORT ( Clk : IN STD_LOGIC ;
```

```
      Clr, EN : IN STD_LOGIC ;
```

```
      BCD3,BCD2,BCD1, BCD0 : BUFFER STD_LOGIC_VECTOR(3  
DOWNT0 0) ) ;
```

```
END BCD_count ;
```

```
ARCHITECTURE Behavior OF BCD_count IS
```

```
BEGIN
```

```
PROCESS (Clk)
```

```
BEGIN
```

```
  IF Clk'EVENT AND Clk = '1' THEN
```

```
    IF Clr = '1' THEN
```

```
      BCD3 <= "0000" ; BCD2 <= "0000" ; BCD1 <= "0000" ; BCD0 <=  
"0000" ;
```

```
    ELSIF EN = '1' THEN
```

```
      IF BCD0 = "1001" THEN
```

```
        BCD0 <= "0000" ;
```

```
      IF BCD1 = "1001" THEN
```

```
        BCD1 <= "0000";
```

```
      IF BCD2 = "1001" THEN
```

```
        BCD2 <= "0000" ;
```

```
      IF BCD3 = "1001" THEN
```

```

        BCD3 <= "0000" ;

    ELSE

        BCD3 <= BCD3 + '1' ;

    END IF ;

    ELSE

        BCD2 <= BCD2 + '1' ;

    END IF ;

    ELSE

        BCD1 <= BCD1 + '1' ;

    END IF ;

    ELSE

        BCD0 <= BCD0 + '1' ;

    END IF ;

END IF ;

END IF;

END PROCESS;

END Behavior ;

```

1 對 4

```

library IEEE;

use IEEE.STD_LOGIC_1164.all;

ENTITY DMUX14 IS
PORT ( X   : IN   STD_LOGIC_vector(1 downto 0);
      Y: IN STD_LOGIC_vector(3 downto 0);
      A,B,C,D: OUT STD_LOGIC_vector(3 downto 0));

```



```
END DMUX14;
```

```
ARCHITECTURE a OF DMUX14 IS
```

```
BEGIN
```

```
    A <= Y when X="00" else "1111";
```

```
    B <= Y when X="01" else "1111";
```

```
    C <= Y when X="10" else "1111";
```

```
    D <= Y when X="11" else "1111";
```

```
END a;
```

4 對 1

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.all;
```

```
ENTITY MUX41 IS
```

```
PORT ( X   : IN   STD_LOGIC_vector(1 downto 0);
```

```
       A,B,C,D: IN STD_LOGIC_vector(3 downto 0);
```

```
       Y: OUT STD_LOGIC_vector(3 downto 0));
```

```
END MUX41;
```

```
ARCHITECTURE a OF MUX41 IS
```

```
BEGIN
```

```
    Y <= A when X="00" else
```

```
        B when X="01" else
```

```
C when X="10" else
```

```
D;
```

```
END a;
```

上數器

```
LIBRARY IEEE;
```

```
USE IEEE.STD_LOGIC_1164.ALL;
```

```
USE IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
ENTITY UP_COUNTER is
```

```
PORT( CLK: IN STD_LOGIC;
```

```
Q : OUT STD_LOGIC_VECTOR(1 DOWNT0 0));
```

```
END UP_COUNTER;
```

```
ARCHITECTURE a OF UP_COUNTER IS
```

```
SIGNAL QN : STD_LOGIC_VECTOR(1 DOWNT0 0);
```

```
BEGIN
```

```
    PROCESS (CLK)
```

```
    BEGIN
```

```
        IF CLK'event AND CLK='1' THEN
```

```
            QN <= QN+1;
```


```
        END IF;
```

```
    END PROCESS;
```

```
    Q<=QN;
```

```
END a;
```

實驗結果:

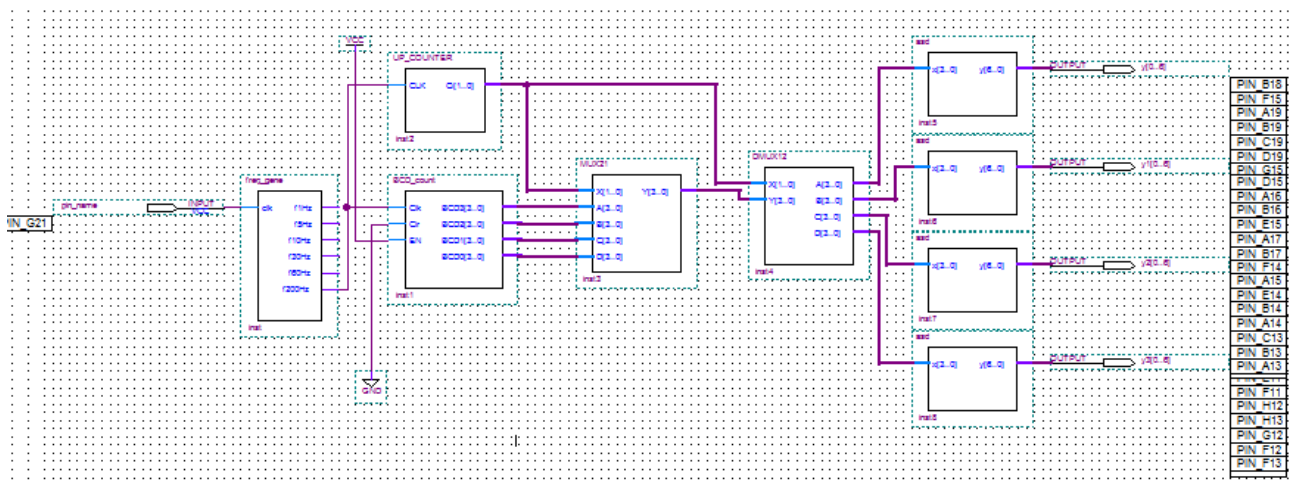

多工掃描 4 位數計數器，200Hz

<https://youtu.be/7ZNZx-hddG4>